Verilog Project

Description: Design a single-cycle RISC-V processor in Verilog that is capable of implementing the RV32I Base Integer Instruction Set except the ***ecall and ebreak*** instructions as given the figure below. Please follow the guidelines in order to receive a proper grade.

RV32I Base Integer Instructions

Inst	Name	FMT	Opcode	funct3	funct7	Description (C)	Note
add	ADD	R	0110011	0x0	0x00	rd = rs1 + rs2	
sub	SUB	R	0110011	0x0	0x20	rd = rs1 - rs2	
xor	XOR	R	0110011	0x4	0x00	rd = rs1 ^ rs2	
or	OR	R	0110011	0x6	0x00	rd = rs1 | rs2	
and	AND	R	0110011	0x7	0x00	rd = rs1 & rs2	
sll	Shift Left Logical	R	0110011	0x1	0x00	rd = rs1 << rs2	
srl	Shift Right Logical	R	0110011	0x5	0x00	rd = rs1 >> rs2	
sra	Shift Right Arith*	R	0110011	0x5	0x20	rd = rs1 >> rs2	msb-extends
slt	Set Less Than	R	0110011	0x2	0x00	rd = (rs1 < rs2)?1:0	
sltu	Set Less Than (U)	R	0110011	0x3	0x00	rd = (rs1 < rs2)?1:0	zero-extends
addi	ADD Immediate	I	0010011	0x0		rd = rs1 + imm	
xori	XOR Immediate	I	0010011	0x4		rd = rs1 ^ imm	
ori	OR Immediate	I	0010011	0x6		rd = rs1 | imm	
andi	AND Immediate	I	0010011	0x7		rd = rs1 & imm	
slli	Shift Left Logical Imm	I	0010011	0x1	imm[5:11]=0x00	rd = rs1 << imm[0:4]	
srli	Shift Right Logical Imm	I	0010011	0x5	imm[5:11]=0x00	rd = rs1 >> imm[0:4]	
srai	Shift Right Arith Imm	I	0010011	0x5	imm[5:11]=0x20	rd = rs1 >> imm[0:4]	msb-extends
slti	Set Less Than Imm	I	0010011	0x2		rd = (rs1 < imm)?1:0	
sltiu	Set Less Than Imm (U)	I	0010011	0x3		rd = (rs1 < imm)?1:0	zero-extends
lb	Load Byte	I	0000011	0x0		rd = M[rs1+imm][0:7]	
lh	Load Half	I	0000011	0x1		rd = M[rs1+imm][0:15]	
lw	Load Word	I	0000011	0x2		rd = M[rs1+imm][0:31]	
lbu	Load Byte (U)	I	0000011	0x4		rd = M[rs1+imm][0:7]	zero-extends
lhu	Load Half (U)	I	0000011	0x5		rd = M[rs1+imm][0:15]	zero-extends
sb	Store Byte	S	0100011	0x0		M[rs1+imm][0:7] = rs2[0:7]	
sh	Store Half	S	0100011	0x1		M[rs1+imm][0:15] = rs2[0:15]	
sw	Store Word	S	0100011	0x2		M[rs1+imm][0:31] = rs2[0:31]	
beq	Branch ==	B	1100011	0x0		if(rs1 == rs2) PC += imm	
bne	Branch !=	B	1100011	0x1		if(rs1 != rs2) PC += imm	
blt	Branch <	B	1100011	0x4		if(rs1 < rs2) PC += imm	
bge	Branch ≥	B	1100011	0x5		if(rs1 >= rs2) PC += imm	
bltu	Branch < (U)	B	1100011	0x6		if(rs1 < rs2) PC += imm	zero-extends
bgeu	Branch ≥ (U)	B	1100011	0x7		if(rs1 >= rs2) PC += imm	zero-extends
jal	Jump And Link	J	1101111			rd = PC+4; PC += imm	
jalr	Jump And Link Reg	I	1100111	0x0		rd = PC+4; PC = rs1 + imm	
lui	Load Upper Imm	U	0110111			rd = imm << 12	
auipc	Add Upper Imm to PC	U	0010111			rd = PC + (imm << 12)	

Important guidelines:

```
module riscv_processor(
   input     clk,

   output [31:0] mem_addr,  // address bus
   output [31:0] mem_wdata, // data to be written
   output [3:0]  mem_wmask, // write mask for the 4 bytes of each word
   input [31:0]  mem_rdata, // input lines for both data and instr
   output    mem_rstrb, // active to initiate memory read (used by IO)
   input     mem_rbusy, // asserted if memory is busy reading value
   input     mem_wbusy, // asserted if memory is busy writing value

   input     reset      // set to 0 to reset the processor
);
```

Processor interface.

1. The tests for the processor design will be automated; therefore, you need to mandatorily implement the interface (given in the figure) in the top module of your design.
2. You can include your own test benches in the submitted files.
3. An example testbench file is attached to demonstrate the purpose of how the design will be tested. Use it only as a reference. Don't depend on the output from this file. Make your own test bench (The attached may not be reliable).
4. Use of the iVerilog (https://steveicarus.github.io/iverilog/) is recommended for testing the Verilog code.
5. Please make sure to name your top_module as *<your_roll_number>_riscv.v* e.g, 20981546_riscv.v